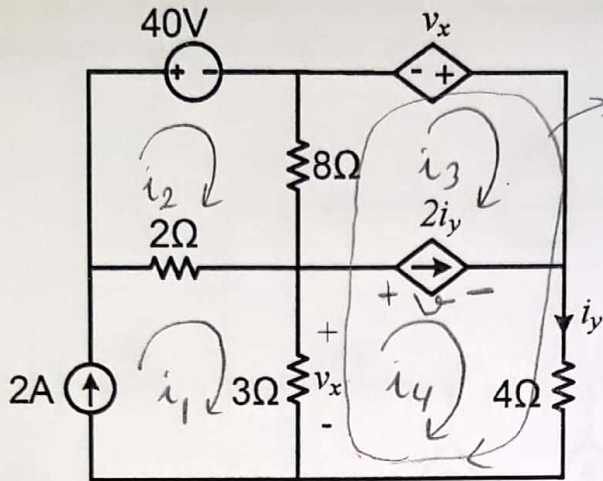


### Question 1 (30 pts)

Find the power supplied by the current controlled current source by using mesh analysis.



super mesh  
After finding mesh currents:  
 $40 + 4(-2) + 3(-2-2) = 0$   
 $40 = 20V$

$$P_{CCCS} = 40 \cdot 2i_y$$

$$= 20 \cdot 2(-2) = -80W$$

dissipated  
+80W supplied

$$\boxed{i_1 = 2A}$$

$$i_4 - i_3 = 2i_y = 2i_4 \Rightarrow \boxed{i_4 = -i_3} \quad (1)$$

KVL in loop 2

$$40 + 8(i_2 - i_3) + 2(i_2 - 2) = 0$$

$$\boxed{10i_2 - 8i_3 = -36} \quad (2)$$

KVL in super mesh

$$-v_x + 4i_4 + 3(i_4 - 2) + 8(i_3 - i_2) = 0$$

$$v_x = 3(i_1 - i_4) = 3(2 - i_4)$$

$$-6 + 3i_4 + 7i_4 + 8i_3 - 8i_2 = 6 \leftarrow \text{Substitute (1)}$$

$$\boxed{-2i_3 - 8i_2 = 12} \quad (3)$$

$$8i_3 = 10i_2 + 36$$

$$= +16$$

$$\boxed{i_3 = +2A} \quad \boxed{i_4 = -2A}$$


$$10i_2 - 8i_3 = -36$$

$$\rightarrow 32i_2 + 8i_3 = -48$$


$$42i_2 = -84 \Rightarrow \boxed{i_2 = -2A}$$
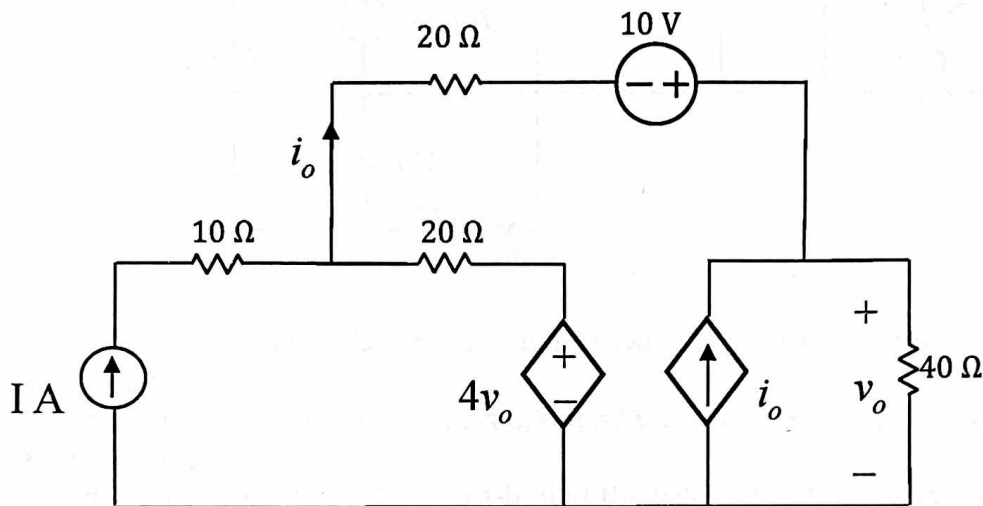
## Question 2 (30 pts)

In the circuit shown below, the independent current source magnitude  $I$  is not known. However, the output voltage  $v_o$  across the  $40\ \Omega$  resistor is measured as  $3\text{ V}$ . Find the corresponding output voltage  $v_o$  when the independent current source magnitude becomes  $2I$  amperes.  
Hint: Superposition principle might be helpful.



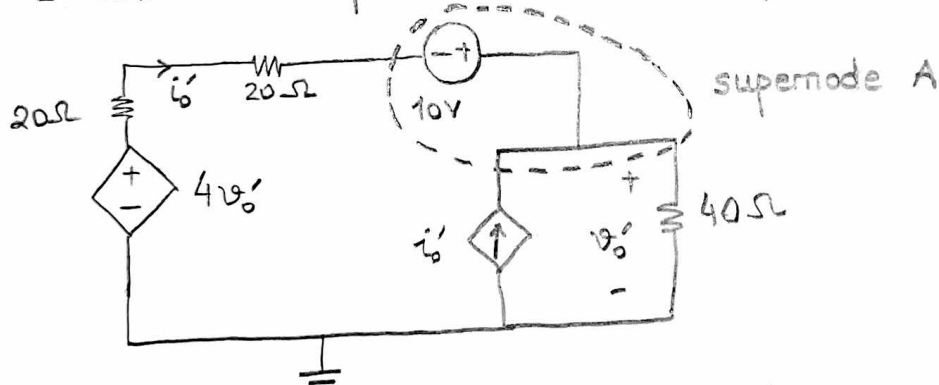- Kill the independent current source, solve for  $v_o'$ :



KCL supernode A:

$$-i_o' - i_o' + \frac{v_o'}{40} = 0 \quad \rightarrow \quad i_o' = \frac{v_o'}{80}$$

constraint equation:

$$\frac{4v_o' - (v_o' - 10)}{20} = i_o' = \frac{v_o'}{80}$$


$$\Rightarrow v_o' = -4\text{ V}$$

$\Rightarrow$  contribution of  $I\text{ A}$  in the output is  $7\text{ V}$ .


$\Rightarrow$  if input were  $2I\text{ A}$ , output  $14\text{ V}$

$$\Rightarrow \text{overall output} \quad -4\text{ V} + 14\text{ V} = \boxed{10\text{ V}}$$


Question 3 (40 pts)

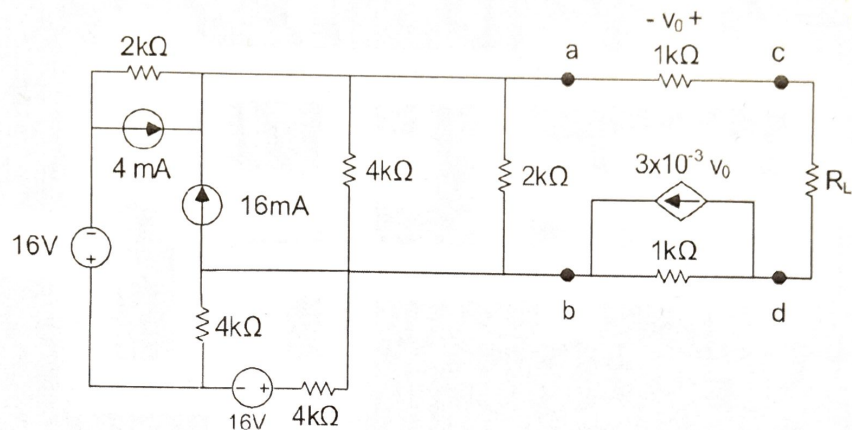

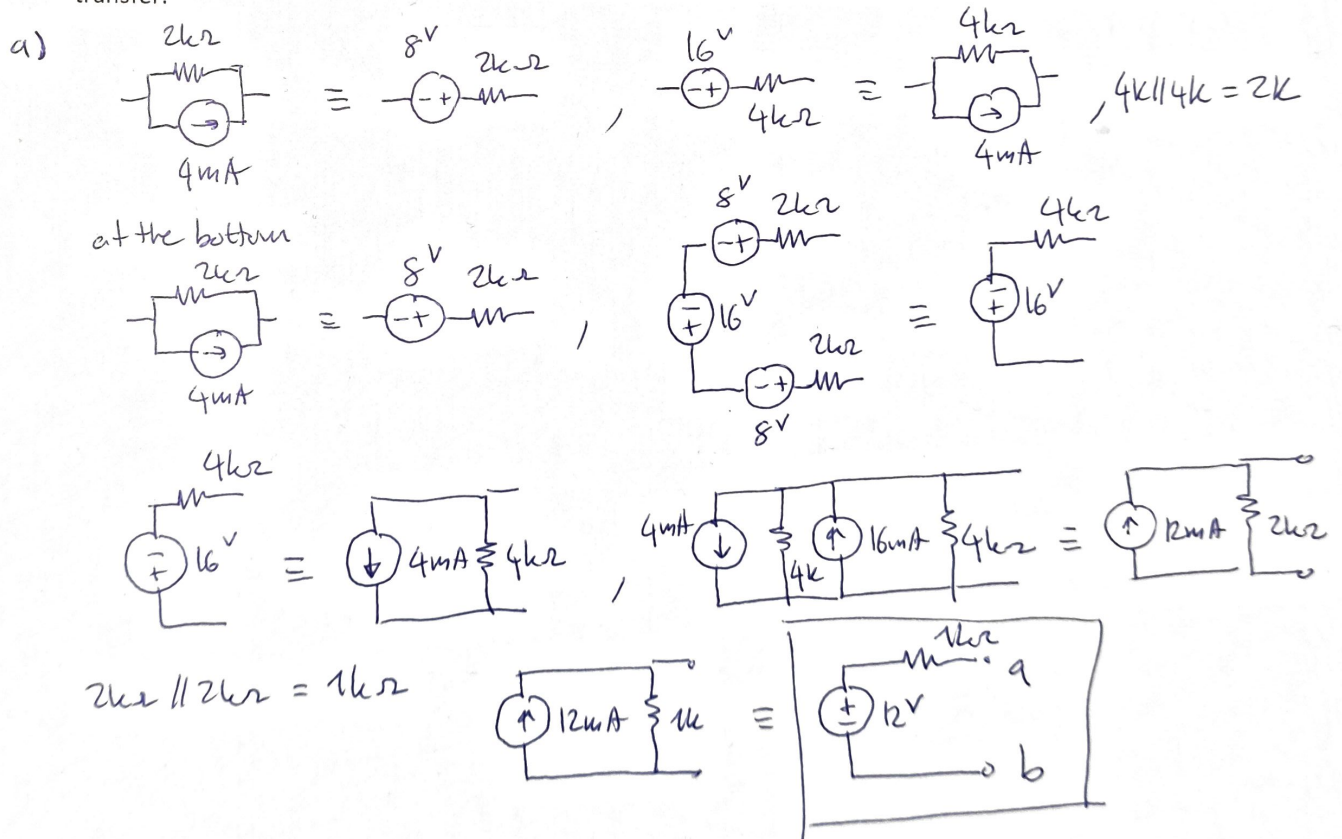- Use source transformations to find the Thevenin Equivalent of the circuit to the left of the terminals a-b.
- Use the equivalent circuit from part-a, to find the next Thevenin equivalent circuit to the left of the terminal c-d.
- Using the equivalent circuit in part-b, find the value of  $R_L$  that could ensure maximum power transfer.




b) Based on a), we have

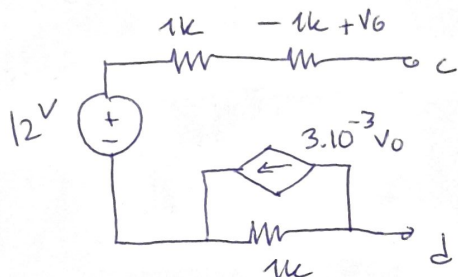

Step 1, Find the open-circuit voltage. Since  $i = 0$  on the top two resistors,  $V_0 = 0$  and hence  $V_{oc} = 12V$

Step 2: Find  $i_{sc}$

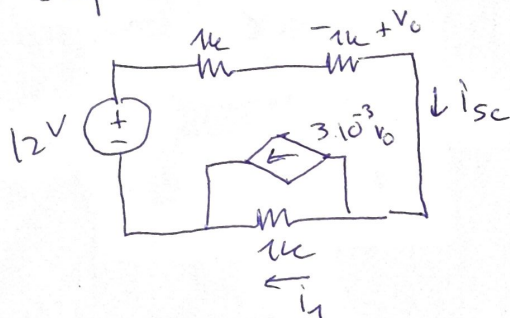

$$V_0 = -1 \times 10^3 i_{sc} \quad (\text{Ohm's law})$$

$$i_1 = -3 \times 10^{-3} V_0 + i_{sc} \quad (\text{KCL})$$


$$= 3 i_{sc} + i_{sc} = 4 i_{sc}$$

$$12 - 2 \times 10^3 i_{sc} - 4 \times 10^3 i_{sc} = 0 \quad (\text{KVL})$$

$$\rightarrow i_{sc} = \frac{12}{6 \times 10^3} = 2 \text{ mA}$$

$$V_{th} = 12V$$
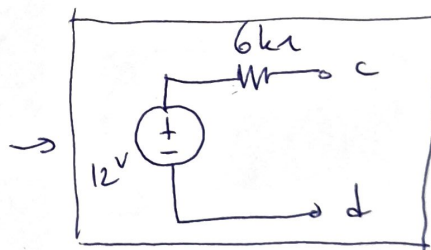
$$R_{th} = \frac{V_{oc}}{i_{sc}} = \frac{12}{2 \times 10^{-3}} = 6 \text{ k}\Omega$$



c)  $R_L = R_{th}$  maximizes power, so  $R_L = 6 \text{ k}\Omega$