
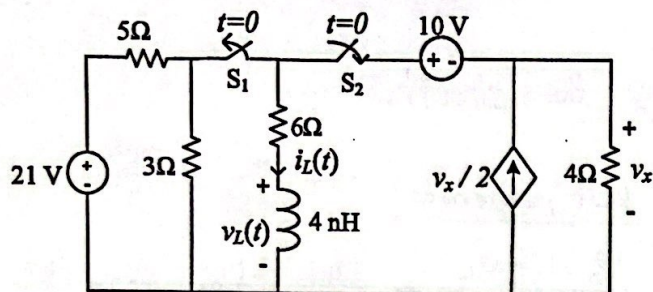

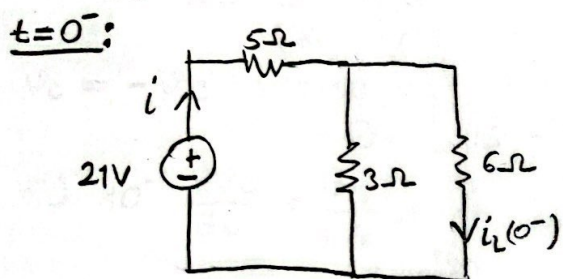
## Question 2 (40 pts)

In the circuit below, switch  $S_1$  is opened at  $t=0$  while switch  $S_2$  is closed at  $t=0$ . Assume DC steady state conditions are established at  $t=0^-$ .




- Find inductor current  $i_L(t)$  at  $t=0^+$ .
- Find the energy stored in the inductor as  $t \rightarrow \infty$ .
- Find  $i_L(t)$  for  $t>0$ .
- Find  $v_x(t)$  for  $t>0$ .



$$R_{eq} = \frac{6 \cdot 3}{6+3} + 5 = 7 \Omega$$

$$i = \frac{21}{7} = 3 \text{ A}$$

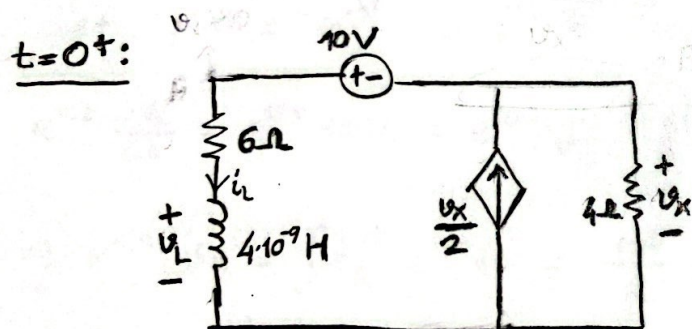
$$i_L(0^-) = 3 \cdot \frac{1}{3} = 1 \text{ A}$$



$$i_L(0^+) = i_L(0^-) = 1 \text{ A}$$

(current of inductor is <sup>always</sup> continuous).

Apply Thevenin:

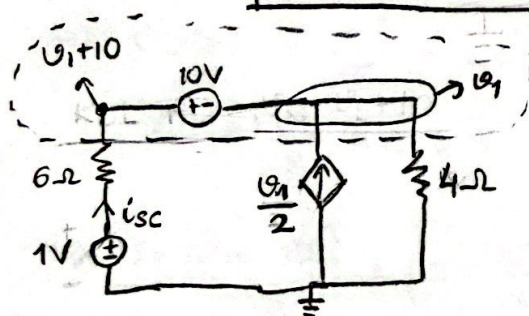


KCL supernode:  $\frac{v_1 + 10 - 1}{6} + \frac{-v_1}{2} + \frac{v_1}{4} = 0$

(2)                      (6)                      (3)

$$\Rightarrow v_1 = 18 \text{ V} \Rightarrow i_{sc} = -\frac{v_1 + 9}{6} = -4.5 \text{ A}$$

$$\Rightarrow R_{Th} = \left| \frac{1}{-4.5} \right| = \frac{2}{9} \Omega$$

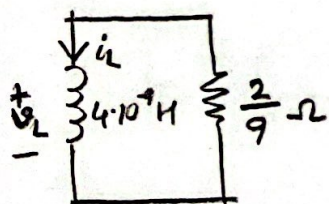Therefore, the Thevenin equivalent circuit is:



$$\text{KVL: } v_L + \frac{2}{9} i_L = 0 \Rightarrow 4 \cdot 10^{-9} \frac{di_L}{dt} + \frac{2}{9} i_L = 0$$

$$\Rightarrow \frac{di_L}{dt} + \frac{10^9}{18} i_L = 0 \Rightarrow \int \frac{di_L}{i_L} = \int \frac{-10^9}{18} dt$$

$$\Rightarrow \ln i_L = \frac{-10^9}{18} t + C \quad (\text{Continues at the next page.})$$