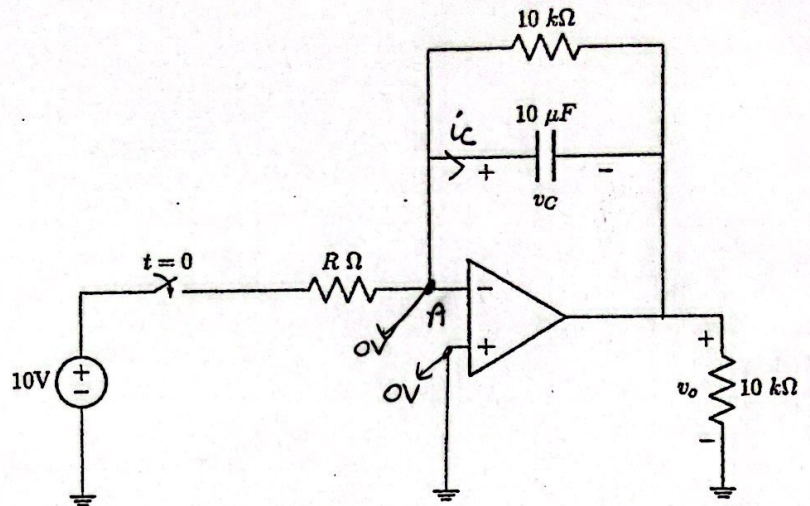


Question 3 (30 pts)

For the circuit on the right, the op-amp is ideal, has infinite gain, and operates in the linear region. The initial capacitor voltage $v_C(0^-) = 5V$. Find the resistor value R , such that $v_o(t) = -10V$ at $t = 0.5$ sec.



$$\text{KCL at A: } \frac{-10}{R} + \frac{-v_o}{10k} + i_C = 0$$

$$i_C = \frac{10}{R} + \frac{v_o}{10k} = 10^{-5} \frac{dv_C}{dt}$$

$$v_o = -v_C \quad \left\{ \text{const eqn.} \right.$$

$$\Rightarrow 10^{-5} \frac{dv_C}{dt} + \frac{v_C}{10k} = \frac{10}{R} \Rightarrow \frac{dv_C}{dt} + 10 v_C = \frac{10^6}{R}$$

Let $\mu(t) = e^{\int 10 dt} = e^{10t}$. Multiply the eqn by $\mu(t)$:

$$e^{10t} \frac{dv_C}{dt} + e^{10t} \cdot 10 v_C = e^{10t} \cdot \frac{10^6}{R} = (e^{10t} \cdot v_C)'$$

$$\Rightarrow e^{10t} \cdot v_C = \int \frac{10^6}{R} e^{10t} dt = \frac{10^5}{R} e^{10t} + C$$

$$\Rightarrow v_C(t) = \frac{10^5}{R} + C e^{-10t}$$

$$v_C(0^-) = \frac{10^5}{R} + C = 5 \Rightarrow C = 5 - \frac{10^5}{R}$$

$$\Rightarrow v_C(t) = \frac{10^5}{R} + \left(5 - \frac{10^5}{R}\right) e^{-10t} = \frac{10^5}{R} (1 - e^{-10t}) + 5 e^{-10t}$$

$$v_o(0.5) = -10V \Rightarrow v_C(0.5) = 10V = \frac{10^5}{R} (1 - e^{-5}) + 5 e^{-5}$$

$$\Rightarrow \frac{10^5}{R} (1 - e^{-5}) = 10 - 5 e^{-5} \Rightarrow \frac{10^5}{R} = \frac{10 - 5 e^{-5}}{1 - e^{-5}}$$

$$\Rightarrow R = 10^5 \frac{1 - e^{-5}}{10 - 5 e^{-5}} \Omega$$