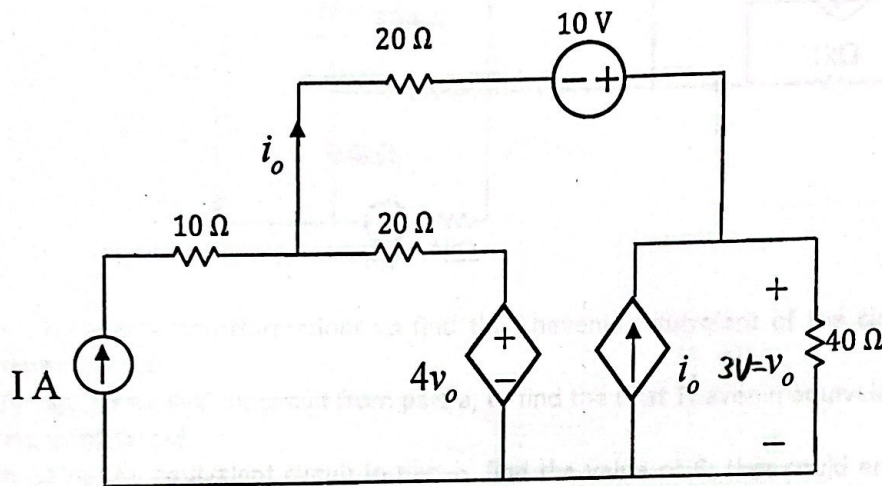



Question 2 (30 pts)

In the circuit shown below, the independent current source magnitude  $I$  is not known. However, the output voltage  $v_o$  across the  $40\ \Omega$  resistor is measured as  $3\text{ V}$ . Find the corresponding output voltage  $v_o$  when the independent current source magnitude becomes  $2I$  amperes.

Hint: Superposition principle might be helpful.



Kill current source:

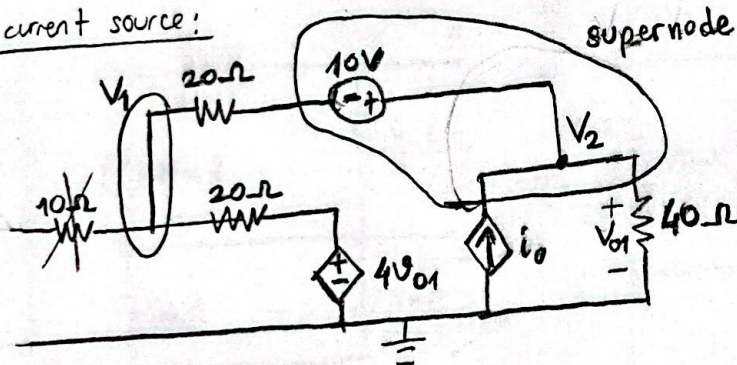

$$\frac{V_1}{10} + \frac{V_1 - 4v_{o1}}{20} + \frac{V_1 - (V_2 - 10)}{20} = 0$$

$$\frac{V_2 - 10 - V_1}{20} + \frac{V_2}{40} = i_o$$

$$\frac{V_2}{40} = v_{o1}, \quad \frac{V_1 - V_2 + 10}{20} = i_o$$

$$\left[ \begin{array}{cc|c} \frac{1}{10} & -\frac{11}{200} & -\frac{1}{2} \\ -\frac{1}{10} & \frac{1}{8} & \frac{1}{2} \end{array} \right] \rightarrow \left[ \begin{array}{cc|c} \frac{1}{10} & -\frac{11}{200} & -\frac{1}{2} \\ 0 & \frac{14}{200} & 0 \end{array} \right] \Rightarrow \left. \begin{array}{l} V_2 = 0\text{ V} \\ V_1 = -5\text{ V} \\ V_{o1} = 0\text{ V} \end{array} \right\} \begin{array}{l} v_o' = v_o + v_{o1} \\ \boxed{= 3\text{ V}} \end{array}$$